
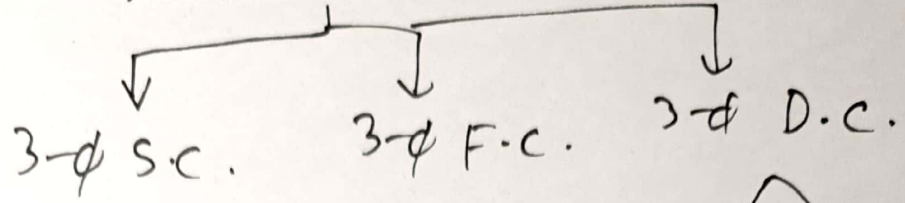


3- ϕ Bridge converters

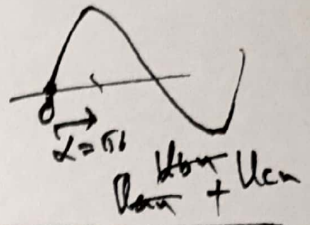



3- ϕ Semi-converter:



Case (a): Let $\alpha \leq \pi/3$ (60°)

Let $\alpha = \pi/6$ (30°)

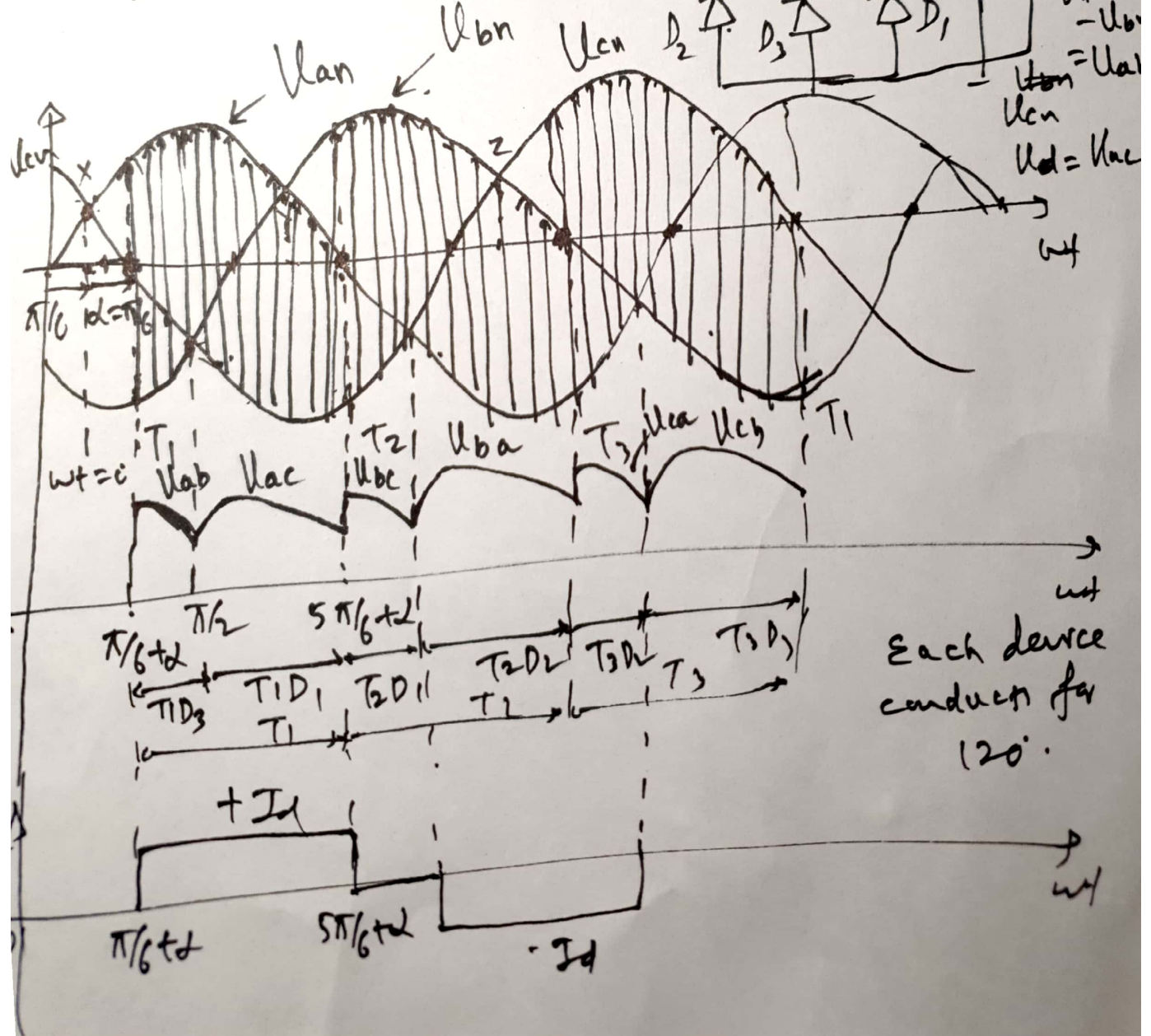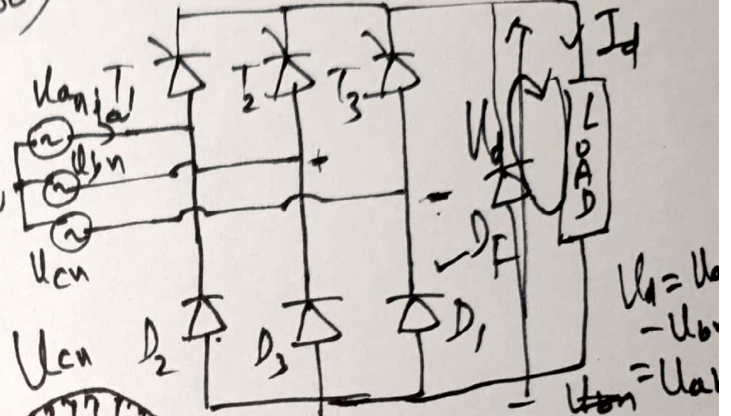$i_a = +I_d$ when T_1 conducts
 $= -I_d$ when D_2 conducts



Expression for converter Average o/p voltage: (2)

Average DC o/p voltage,

$$V_d = \frac{1}{2\pi/3} \left\{ \int_{\pi/6+\alpha}^{\pi/2} V_{ab} d(\omega t) + \int_{\pi/2}^{5\pi/6+\alpha} V_{ac} d(\omega t) \right\}$$

Let $V_{an} = V_m \sin \omega t$

$V_{bn} = V_m \sin(\omega t - 2\pi/3)$ &

$V_{cn} = V_m \sin(\omega t + 2\pi/3)$

$\therefore V_{ac} = V_{an} - V_{cn} = V_m \sin \omega t - V_m \sin(\omega t + 2\pi/3)$

$V_{ac} = V_m \left[\sin \omega t - \sin \omega t \cos 120^\circ - \cos \omega t \sin 120^\circ \right]$

$= V_m \left[\sin \omega t + \frac{1}{2} \sin \omega t - \frac{\sqrt{3}}{2} \cos \omega t \right]$

$= V_m \left[\frac{3}{2} \sin \omega t - \frac{\sqrt{3}}{2} \cos \omega t \right]$

$\Rightarrow V_{ac} = \sqrt{3} V_m \sin(\omega t - \pi/6)$

By, $V_{ab} = V_{an} - V_{bn} = \sqrt{3} V_m \sin(\omega t + \pi/6)$

$$\therefore V_d = \frac{3}{2\pi} \left\{ \int_{\pi/6+\alpha}^{\pi/2} \sqrt{3} V_m \sin(\omega t + \pi/6) d(\omega t) + \int_{\pi/2}^{5\pi/6+\alpha} \sqrt{3} V_m \sin(\omega t - \pi/6) d(\omega t) \right\}$$

$$\Rightarrow V_d = \frac{3\sqrt{3} V_m}{2\pi} \left\{ \left| -\cos(\omega t + 30^\circ) \right|_{90^\circ}^{\pi/6+\alpha} + \left| -\cos(\omega t - 30^\circ) \right|_{90^\circ}^{150^\circ+\alpha} \right\}$$


$$= \frac{3\sqrt{3} V_m}{2\pi} \left\{ -\cos(120^\circ) + \cos(60^\circ + \alpha) - \cos(120^\circ + \alpha) + \cos(60^\circ) \right\}$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \left\{ \frac{1}{2} + \cos 60^\circ \cos \alpha - \sin 60^\circ \sin \alpha - \cos 120^\circ \cos \alpha + \sin 120^\circ \sin \alpha + \cos 60^\circ \right\}$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \left\{ \frac{1}{2} + \frac{1}{2} \cos \alpha - \frac{\sqrt{3}}{2} \sin \alpha + \frac{1}{2} \cos \alpha + \frac{\sqrt{3}}{2} \sin \alpha + \frac{1}{2} \right\}$$

$$V_d = \frac{3\sqrt{3}V_m}{2\pi} [1 + \cos\alpha]$$
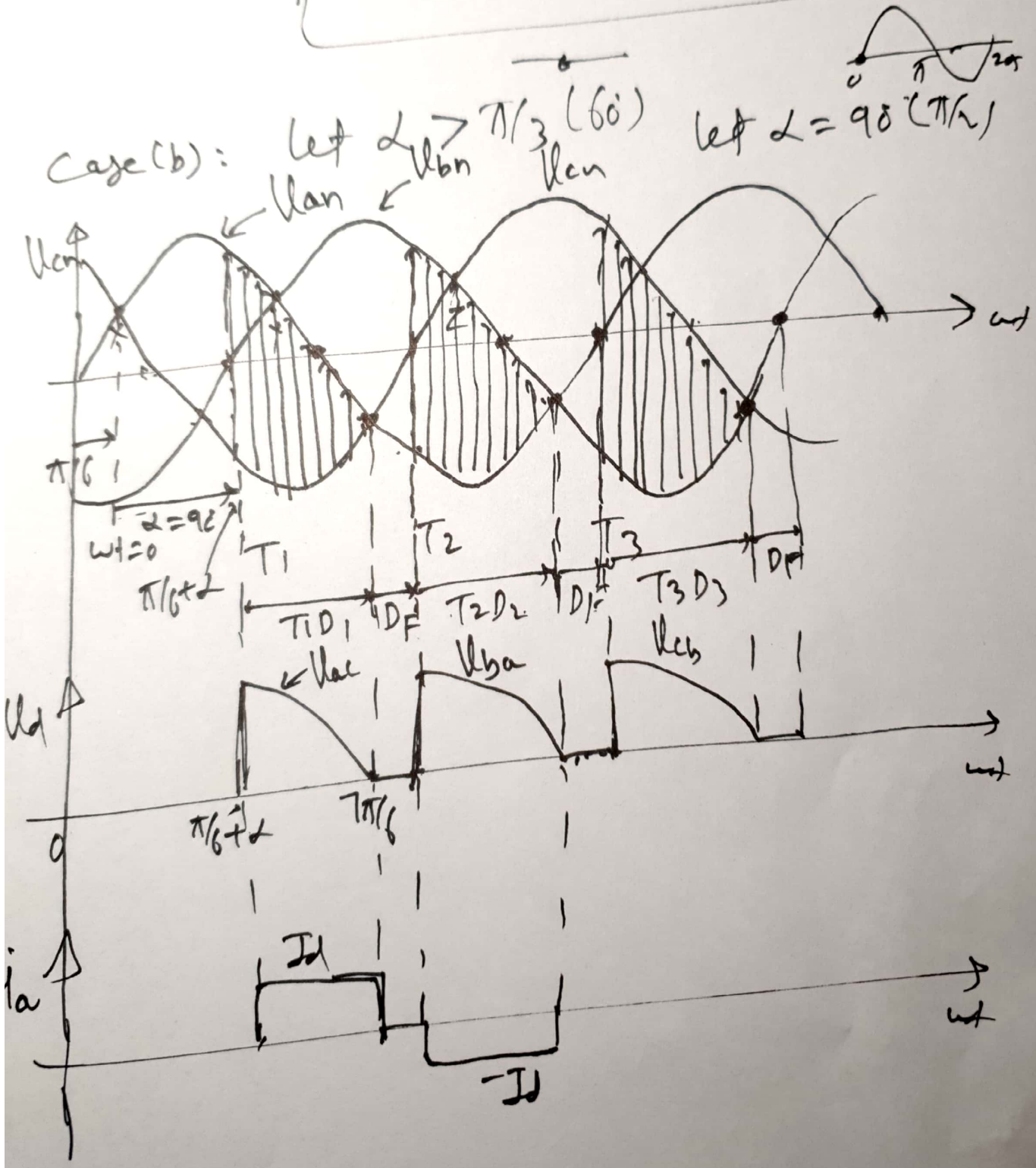
$$\text{For } \alpha = 0, V_{d0} = \frac{3\sqrt{3}V_m}{\pi}$$



Convertex Average o/p voltage,

$$V_d = \frac{1}{2\pi/3} \int_{\pi/6}^{7\pi/6} v_{ac} d(\omega t) = \frac{3}{2\pi} \int_{\pi/6}^{7\pi/6} \sqrt{3} V_m \sin(\omega t - \pi/6) d(\omega t)$$


$$V_d = \frac{3\sqrt{3} V_m}{2\pi} \int_{\alpha+3i}^{210} \sin(\omega t - 3i) d(\omega t)$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \left[-\cos(\omega t - 3i) \right]_{\alpha+3i}^{210}$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \left[-\cos(210 - 3i) + \cos(\alpha + 3i - 3i) \right]$$

$$= \frac{3\sqrt{3} V_m}{2\pi} \left[-\cos 180 + \cos \alpha \right]$$
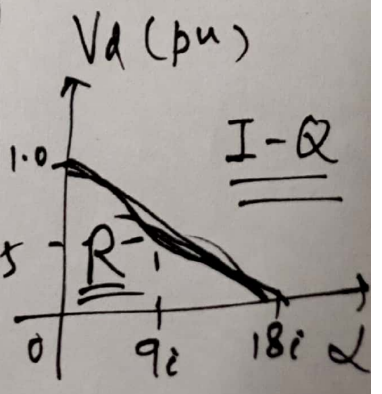
$$\Rightarrow V_d = \frac{3\sqrt{3} V_m}{2\pi} (1 + \cos \alpha)$$



For \$\alpha = 0\$, \$V_d = \frac{3\sqrt{3} V_m}{\pi} = 1.0 \text{ pu}\$

For \$\alpha = 90\$, \$V_d = \frac{3\sqrt{3} V_m}{2\pi} = \frac{1}{2}\$

For \$\alpha = 180\$, \$V_d = 0\$

\$= 0.5 \text{ pu}\$

$$\text{Case (a)} : \alpha < \pi/3$$

$$\text{Case (b)} : \alpha > \pi/3$$

$$\alpha = \pi/3$$

Home Assignment