

Tutorial - 2

(Basic Laws & Theorems) - 1

P2.1 In the circuit configuration of Fig P2.1 determine the voltage drop across each element as well as the power dissipated. All the resistances are in ohms.

$$[V_{10\Omega} = 18V, V_{9\Omega} = 24V, V_{5\Omega} = 6V, V_{15\Omega} = 18V]$$

$$[P = 32.4W, P = 14.4W, P = 7.2W, P = 21.6W]$$

P2.2 In the configuration of Fig P2.2, find the value of E which permits a power dissipation of $180W$ in the 20Ω resistor. All resistances are in ohms. [165V]

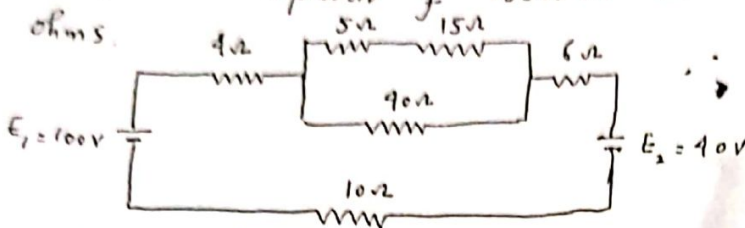


Fig P2.1

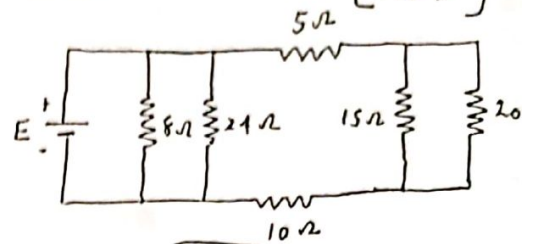


Fig P2.2

P2.3 Find the voltage appearing across the 18Ω resistor in the network of Fig P2.3. [15V]

P2.4 In the circuit of Fig P2.4 find the value of R . [7Ω]

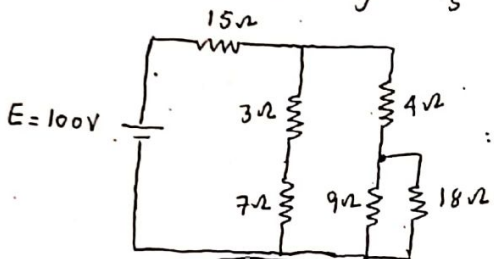


Fig P2.3


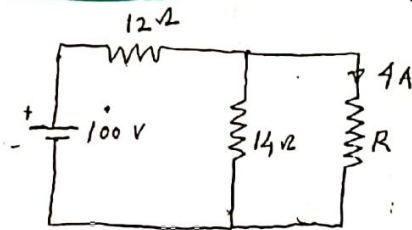


Fig P2.4

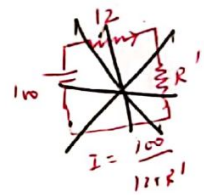

P2.5 In Fig P1.2 compute the voltage required between terminals ab so that a voltage drop of $45V$ occurs across 15Ω resistor. [40V]

P2.6 In the circuitry of Fig P1.1 determine

- (a) the voltage needed across ab so that the voltage drop occurs the 15Ω resistor is $45V$
- (b) the corresponding voltage across the 8Ω resistor for this condition. [150V, 40V]

resistance methods

$[I_A = \frac{5}{3} A, I_B = \frac{10}{3} A, I_C = 2.5 A, I_D = 1.25]$

using the voltage division rule, calculate V_1 and V_2 in Fig P2.8

$[11.39 V, -73.07 V]$

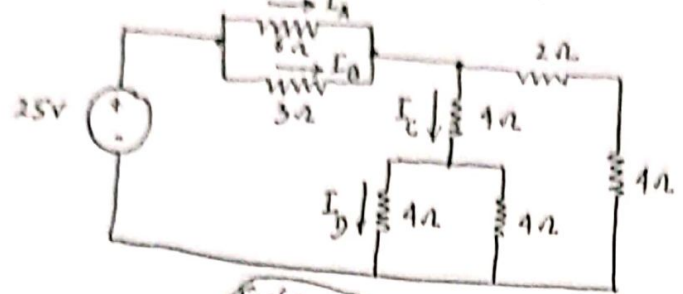


Fig P2.7

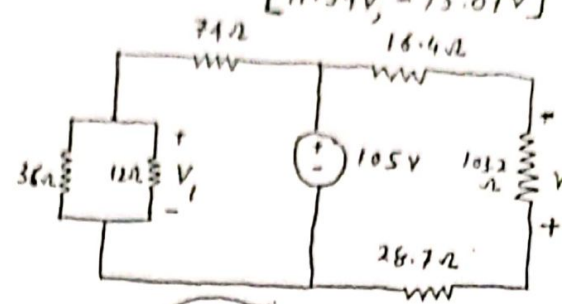


Fig P2.8

P2.9

In Fig P2.9, both ammeters indicate 1.70A. The source supplies 300W. Find R_1 and R_2 .

$[23.9 \Omega, 443 \Omega]$

P2.10

Find the power delivered by the current source in Fig P2.10

$[228 W]$

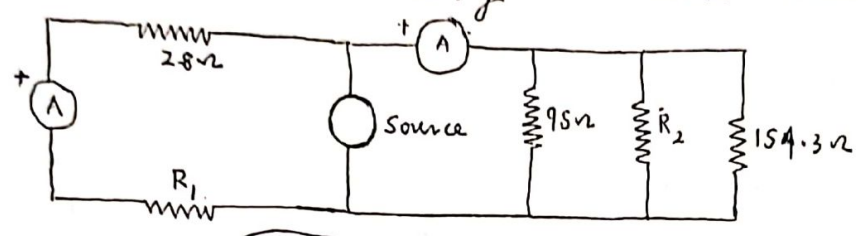


Fig P2.9

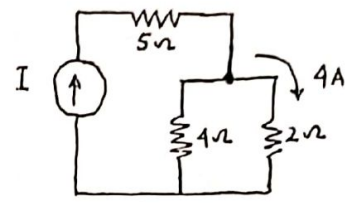


Fig P2.10

P2.11

In the circuit shown in Fig P2.11, find the power absorbed by the 5-V battery.

$[-5 W]$

P2.12

Obtain the current I_x in the 10-Ω resistor in Fig P2.12, using Superposition.

$[-1 A]$

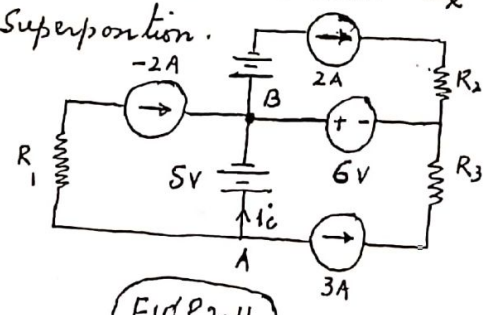


Fig P2.11

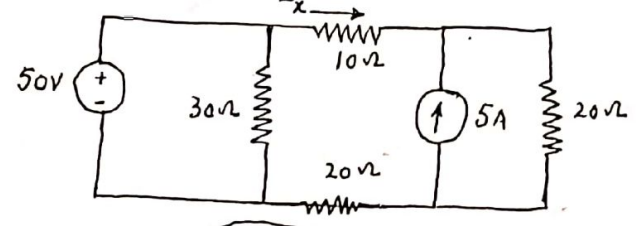


Fig P2.12

P2.13

using superposition, find I in Fig P2.13

$[16.2 A]$

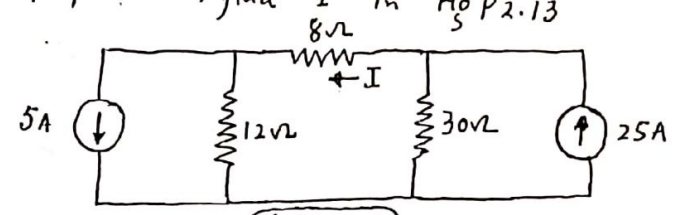


Fig P2.13

for the circuit of Fig P2.14

find the current and power dissipation in each resistor of the circuit shown in Fig P2.15

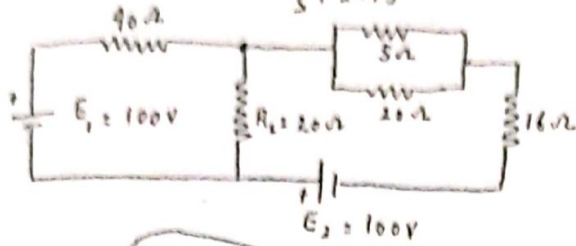


Fig P2.14

in each resistor of the circuit
 $[I_{90} = 0.91A, E_{50} = 0.33A, I_{130} = 0.33A]$
 $P_{90} = 17.4W, P_{50} = 5.56W, P_{130} = 14.44W$



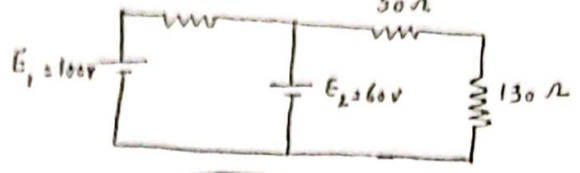


Fig P2.15

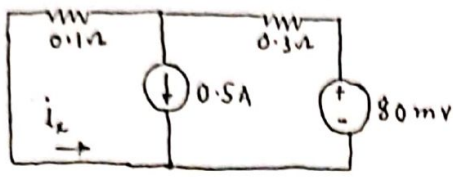
P2.16 Use Superposition to find i_x in each of the circuits shown in Fig



(a)

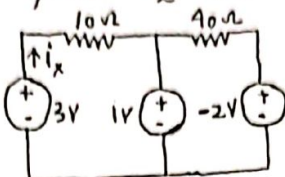

(b)

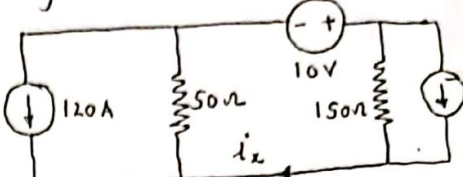

(c)

Fig P2.16

$[-175mA, 200mA, 50mA]$

P2.17 Use the Superposition theorem on the circuits shown in Fig P2.17 to find i in each case.

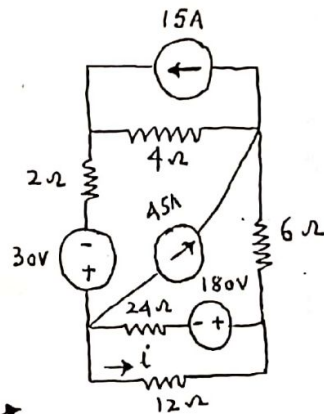
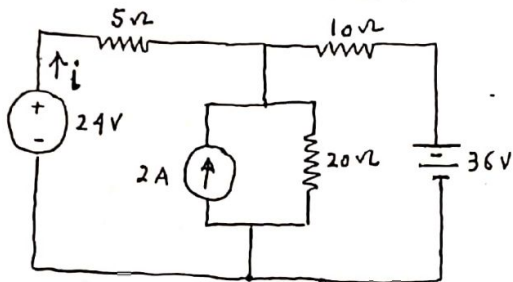


Fig P2.17

$[-1.142A, -9A]$

P2.18 Replace the active network to the left of terminals ab in Fig P. by a Thevenin's equivalent. $[80V, 50\Omega]$

P2.19 Replace the circuit in Fig P2.19 with its Norton's equivalent

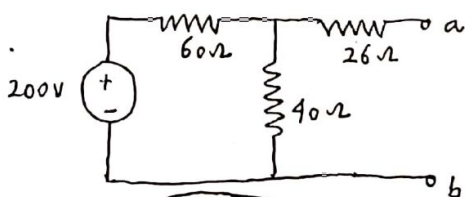


Fig P2.18

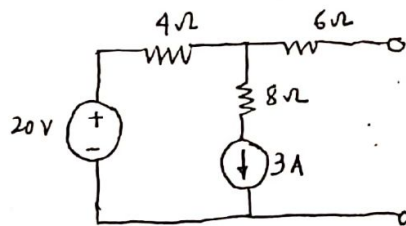


Fig P2.19

$[0.8A, 10\Omega]$

10/6/19

... that will receive maximum power. Determine the value of this maximum power

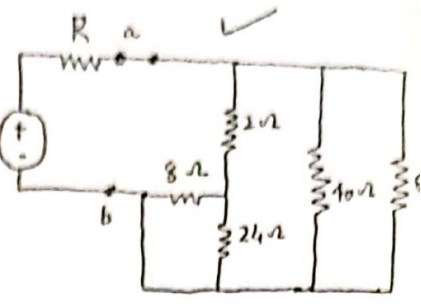
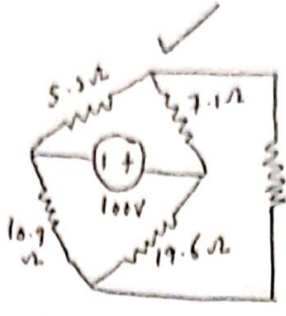


Fig P 2.20

- $12\Omega, 0.75W$
- $10\Omega, 1.09W$
- $6\Omega, 4.167W$

P2.21 Determine the Thevenin's and Norton's equivalent circuits as seen at the terminals a-b for the network of Fig P 2.21. $[32V, 4\Omega, 8A]$

P2.22 For the circuit of Fig P 2.22, find the current flowing through $R = 10\Omega$, using Thevenin's theorem $[0.695A]$

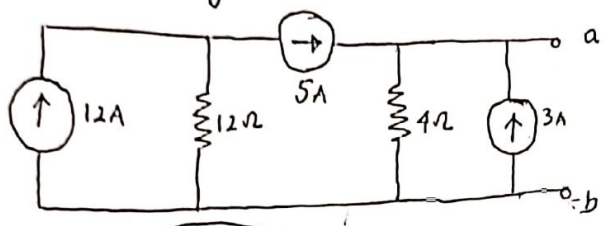


Fig P 2.21

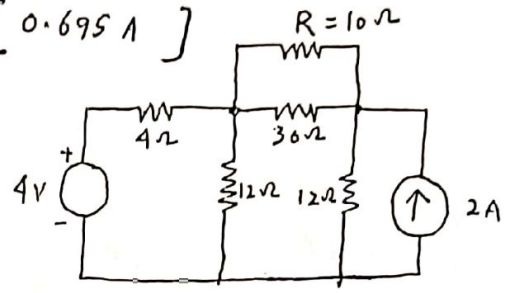


Fig P 2.22

P2.23 A circuit has an arrangement of circuit elements as depicted in Fig P 2.23.

- a) Find the Thevenin's equivalent circuit considering R_4 as the variable load resistance.
- b) Find the current through R_4 when it has values of $\frac{4}{7}\Omega$ and $\frac{40}{7}\Omega$. $[(30V, \frac{20}{7}\Omega), 8.75A, 3.5A]$

P2.24 Assuming R_L in Fig P 2.24 is the load resistor, find the Thevenin's equivalent circuit. $[130V, 22\Omega]$

P2.25 Use Thevenin's theorem to replace the three-loop circuit of Fig P 2.25 by a single loop equivalent circuit in which the identity of R_L is preserved

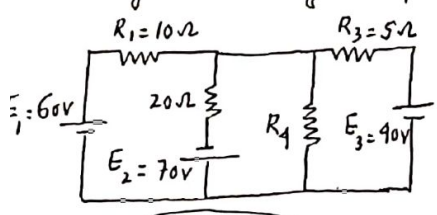


Fig P 2.23

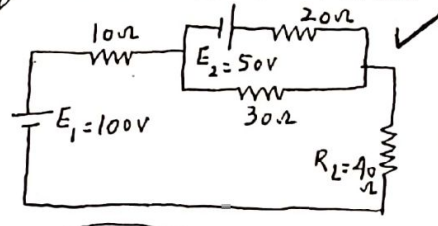


Fig P 2.24

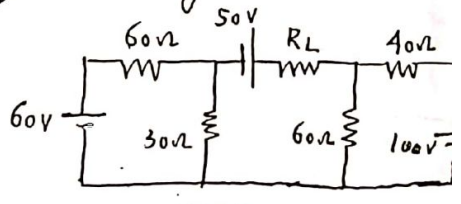


Fig P 2.25

- $[10V, 44\Omega]$